

convolution + phasors = Fourier

Let's see what happens when we put a single unit phasor through an LTI system

$$x(t) = e^{j\omega t} \rightarrow \boxed{h(t)} \rightarrow y(t) \quad y(t) = x(t) * h(t)$$


or, by commutative property

$$\leftarrow y(t) = h(t) * x(t)$$


Fourier Analysis!

$$y(t) = \int_{-\infty}^{+\infty} h(\tau) x(t-\tau) d\tau$$
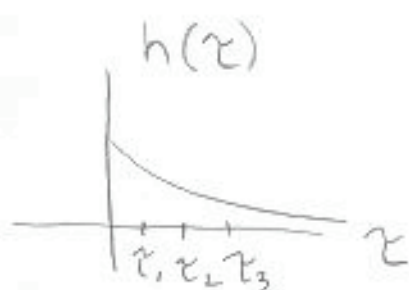
$$y(t) = \int_{-\infty}^{+\infty} h(\tau) e^{j\omega(t-\tau)} d\tau = e^{j\omega t} \underbrace{\int_{-\infty}^{+\infty} h(\tau) e^{-j\omega\tau} d\tau}_{\text{single complex number } H(\omega)}$$



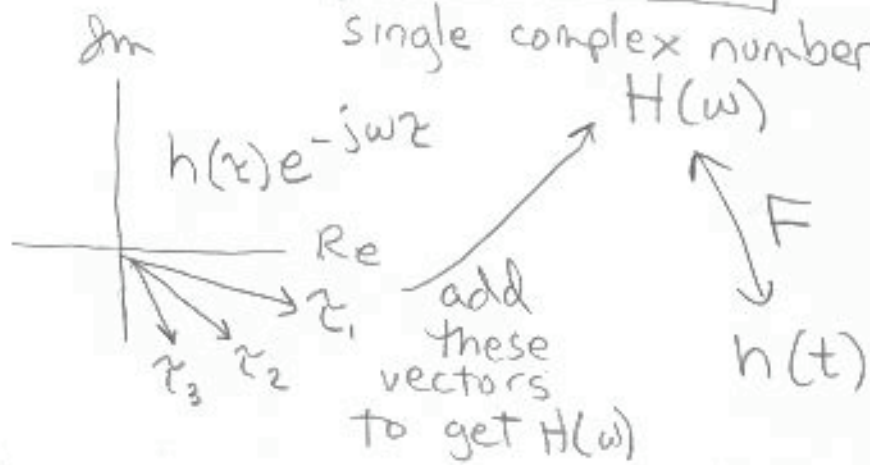if $x(t) = e^{j\omega t}$
 $y(t) = e^{j\omega t} H(\omega)$



Since any $x(t) = \int_{-\infty}^{+\infty} X(\omega) e^{j\omega t} d\omega$ is just the weighted sum of a bunch of phasors, therefore

$$Y(\omega) = X(\omega) H(\omega)$$

Each phasor in the output is a scaled and shifted version of the phasor in the input.


multiplication

$$x(t)y(t) \xleftrightarrow{F} \frac{1}{2\pi} X(\omega) * Y(\omega)$$

Example
AM Radio




$X(\omega)$ = audio signal

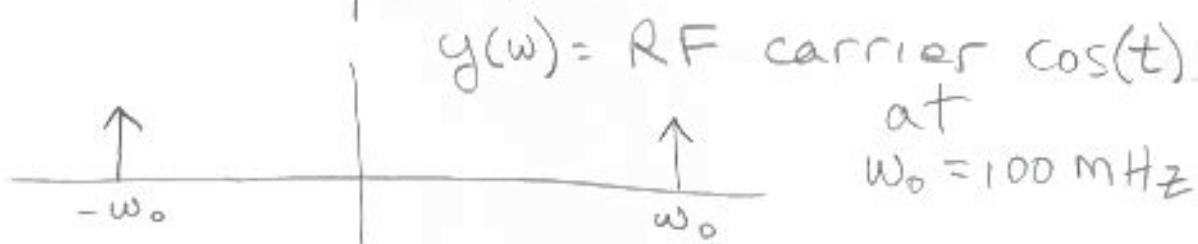

$y(\omega)$ = RF carrier $\cos(t)$
at
 $\omega_0 = 100 \text{ MHz}$

Transmitted
Signal

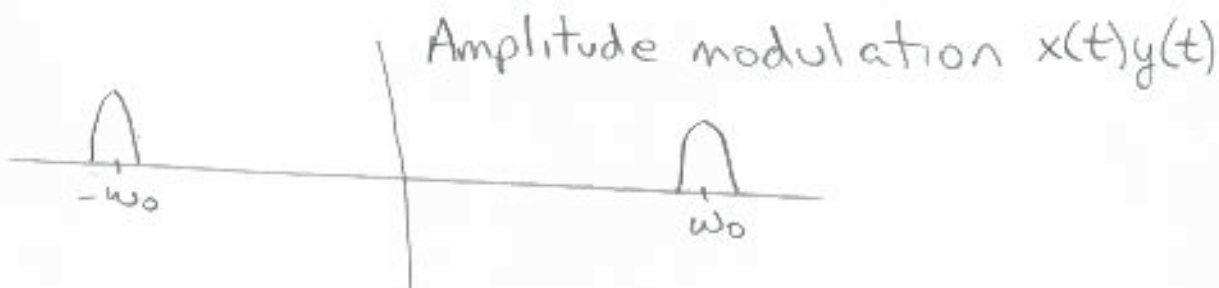

Demodulate by multiplying again by $y(t) = \cos(t)$







eg. first stage of MR scanner

Duality Property

Schaum (eq 5.54)
(prob 5.18)

$$X(t) \xleftrightarrow{F} 2\pi x(-\omega)$$


so, except for coefficients
↙ Either $x(t)$ or $X(\omega)$ ↘

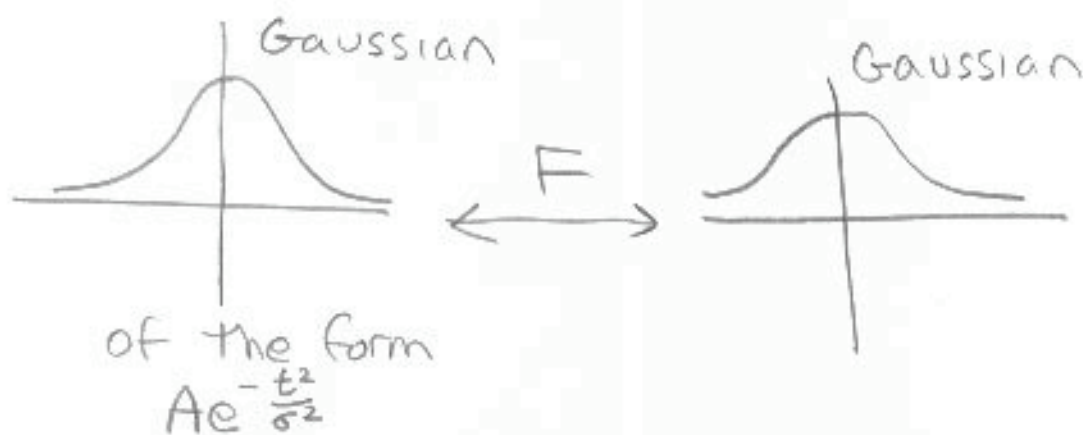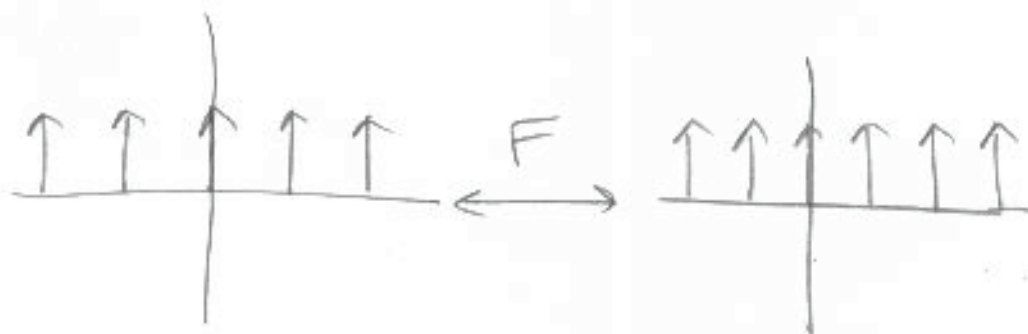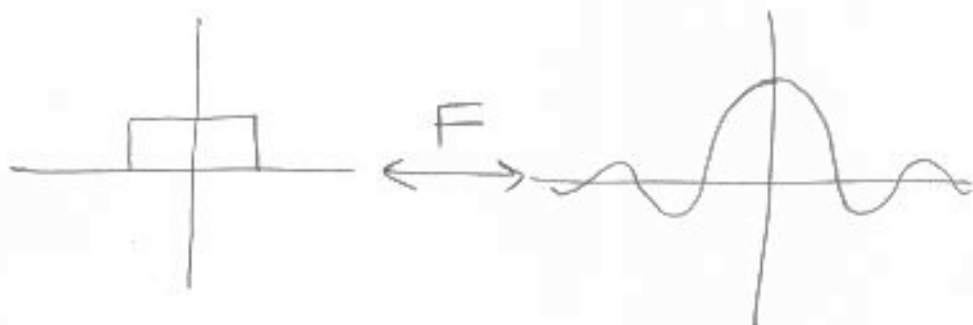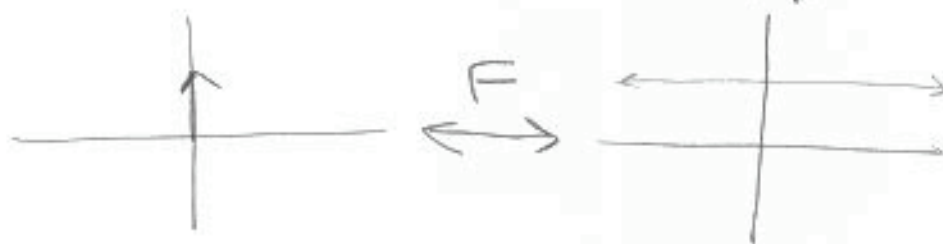

(prob 5.43)

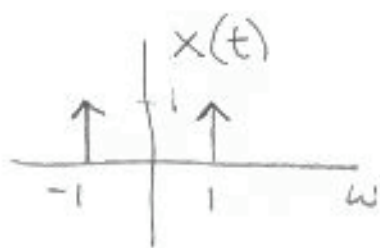EXAMPLE

$x(t) = \delta(t-1) + \delta(t+1)$, what is $X(\omega)$?




$$X(\omega) = \int_{-\infty}^{+\infty} x(t) e^{-j\omega t} dt$$

$$X(\omega) = \left[\int_{-\infty}^{+\infty} \delta(t-1) e^{-j\omega t} dt + \int_{-\infty}^{+\infty} \delta(t+1) e^{-j\omega t} dt \right]$$

$$X(\omega) = \left[e^{-j\omega} + e^{j\omega} \right] = 2 \cos(\omega)$$




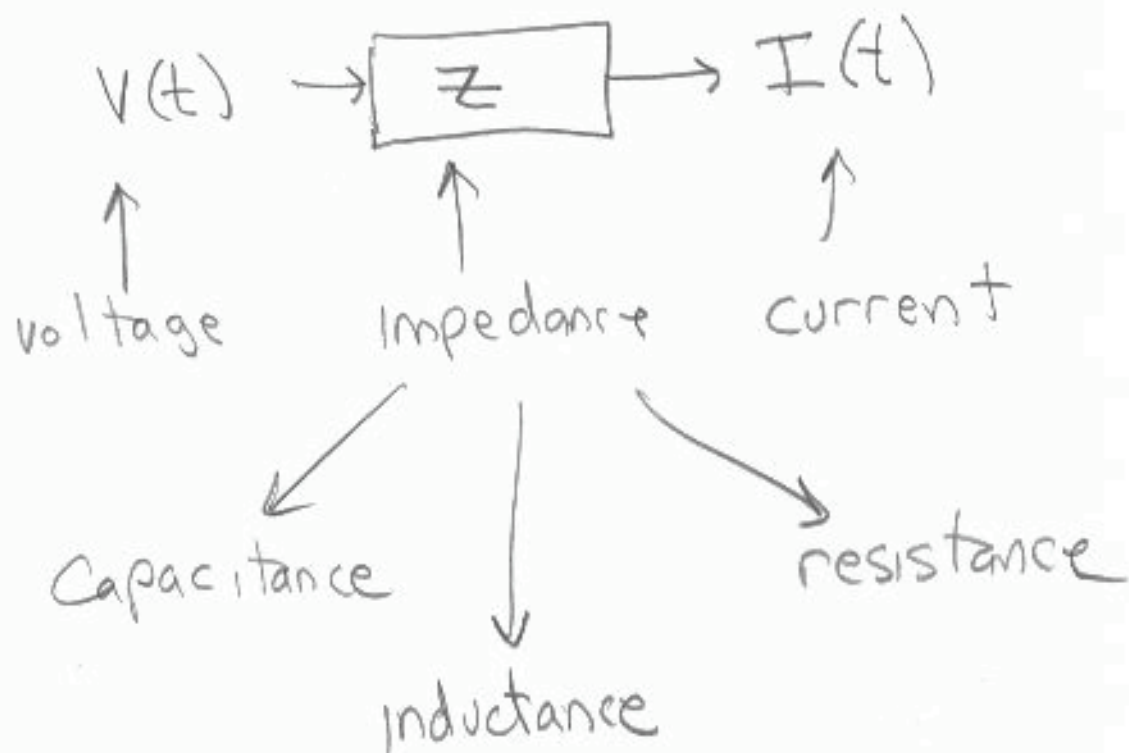Now Consider the electrical impedance of a component as an LTI system



Complex impedance Z
replaces resistance R (which is real)

$$I_C(t) = C \frac{dV_C(t)}{dt}$$

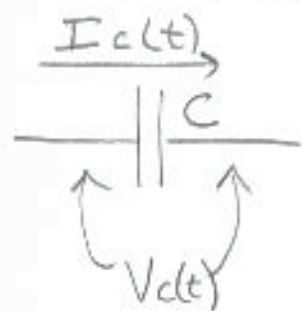

$$\text{if } V_C(t) = e^{j\omega t}$$

$$\text{then } I_C = j\omega C e^{j\omega t}$$

Complex Impedance using Ohms Law


$$Z_C = \frac{V_C(t)}{I_C(t)} = \frac{e^{j\omega t}}{j\omega C e^{j\omega t}} = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

Like wise for a coil

$$V_L(t) = L \frac{dI_L(t)}{dt}$$

$$\text{if } I_L(t) = e^{j\omega t}$$

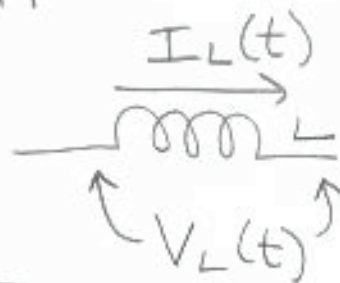
$$\text{then } V_L = j\omega L e^{j\omega t}$$



Complex impedance

$$Z_L = \frac{V_L(t)}{I_L(t)} = \frac{j\omega L e^{j\omega t}}{e^{j\omega t}} = j\omega L$$

what is complex impedance of resistor

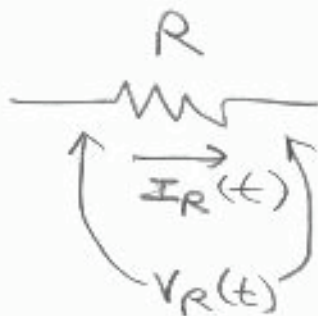

$$V_R(t) = e^{j\omega t}$$

$$I_R(t) = \frac{e^{j\omega t}}{R}$$

$$Z_R = R \quad \text{pure } \underline{\text{real}}$$

Inductance or capacitance is called
"reactance", pure imaginary

impedance of circuits



"complex" impedance
of R is just
a real number

time constant

$$Z = \frac{1}{j\omega C} + R = \frac{1 + j\omega RC}{j\omega C}$$

$$Z = R \quad \left| \omega \gg \frac{1}{RC} \right. \quad \text{"High Pass"}$$

$$Z = \frac{1}{j\omega C} \quad \left| \omega \ll \frac{1}{RC} \right.$$




time constant

$$Z = j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C}$$

$$Z = 0 \quad \left| \quad \omega = \frac{1}{\sqrt{LC}} \quad \text{Resonance} \right.$$

at resonance
impedances
add up
to 0

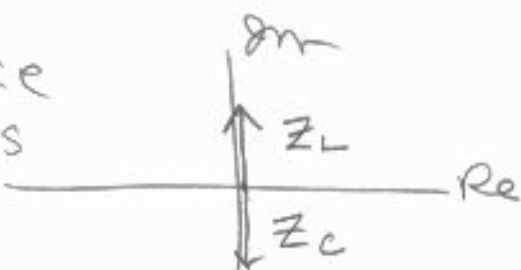

pure "reactance"

add resistance, damps the pendulum




$$Z = j\omega L + \frac{1}{j\omega C} + R =$$

$$\frac{1 - \omega^2 LC}{j\omega C} + R =$$

$$j\left(\frac{\omega^2 LC - 1}{\omega C}\right) + R$$

pure imaginary

pure Real

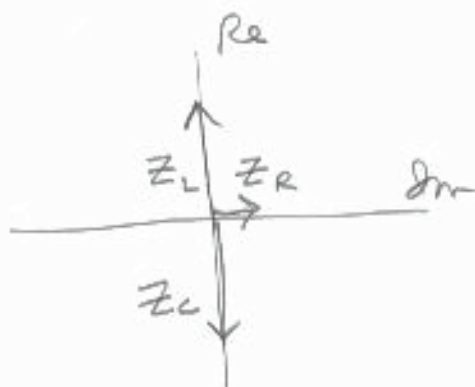

can never
equal zero